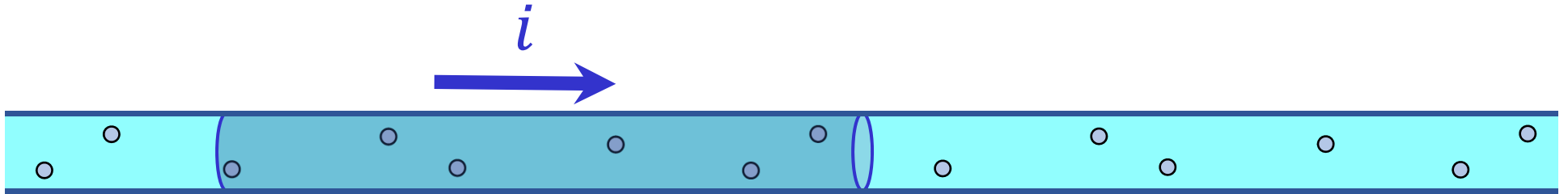


Basic Introduction to Electronics






Electrical current

Symbol: i

Unit: Ampere (A)

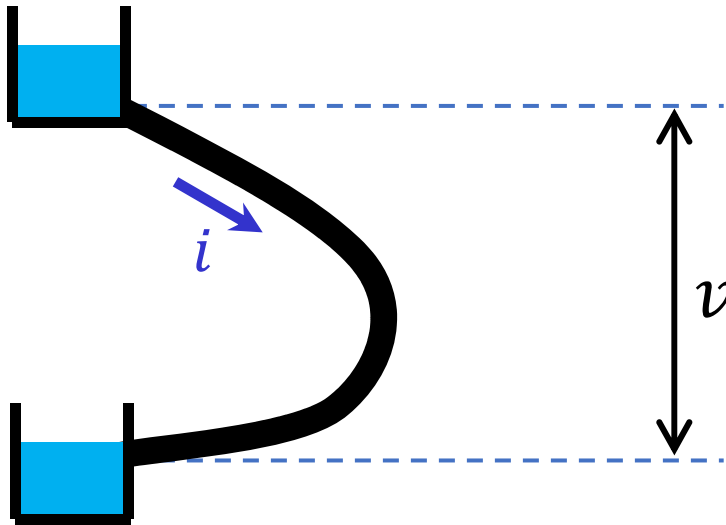For example: $1 \text{ mA} = 0.001 \text{ Amperes}$




Voltage




Symbol: v

Unit: Volt (V)

For example: 5 V


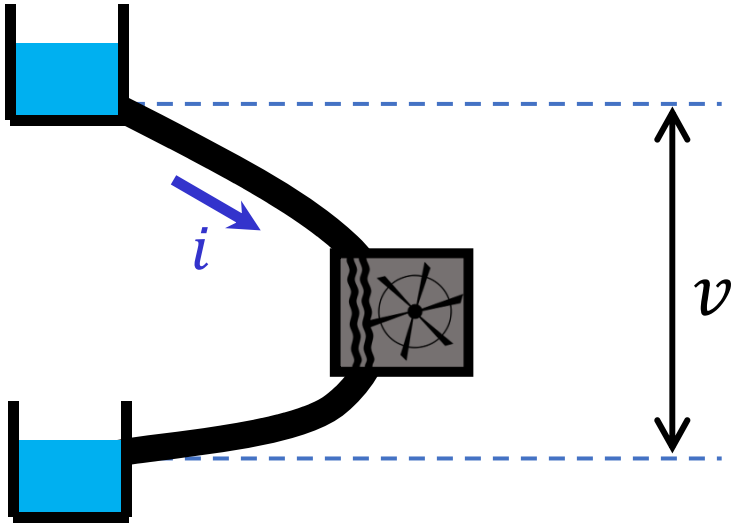


Circuit elements

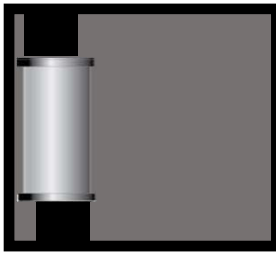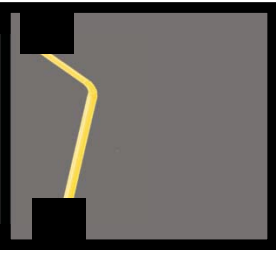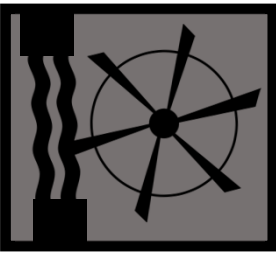


Same v


Different i

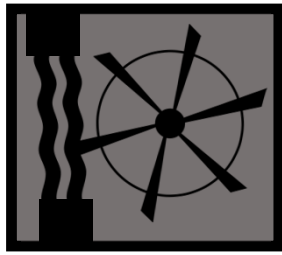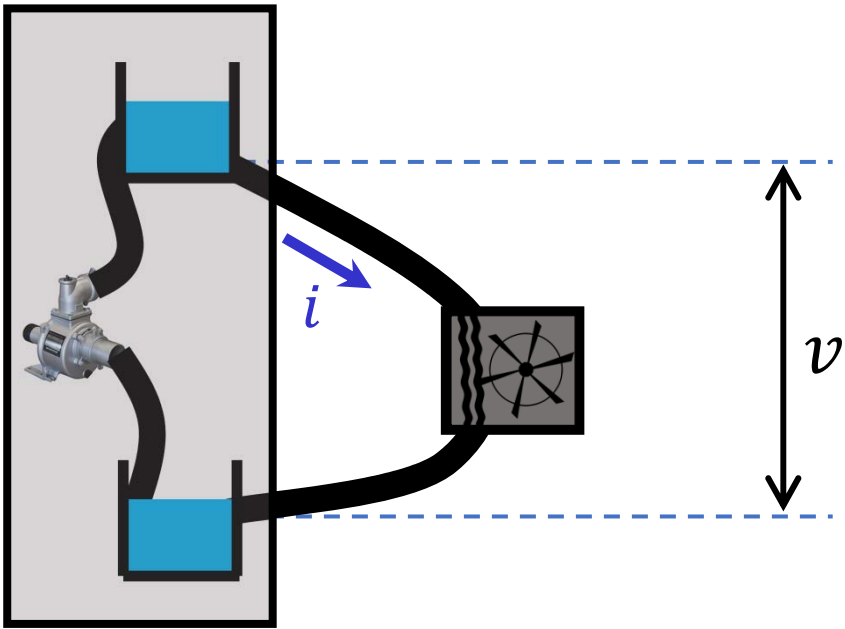


Same v

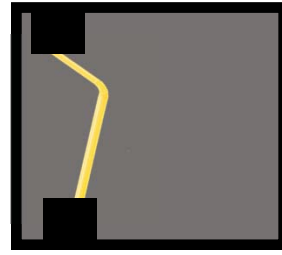

Different i

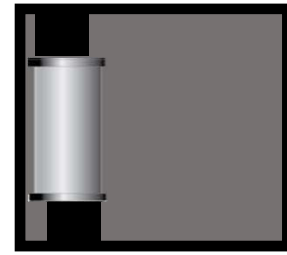


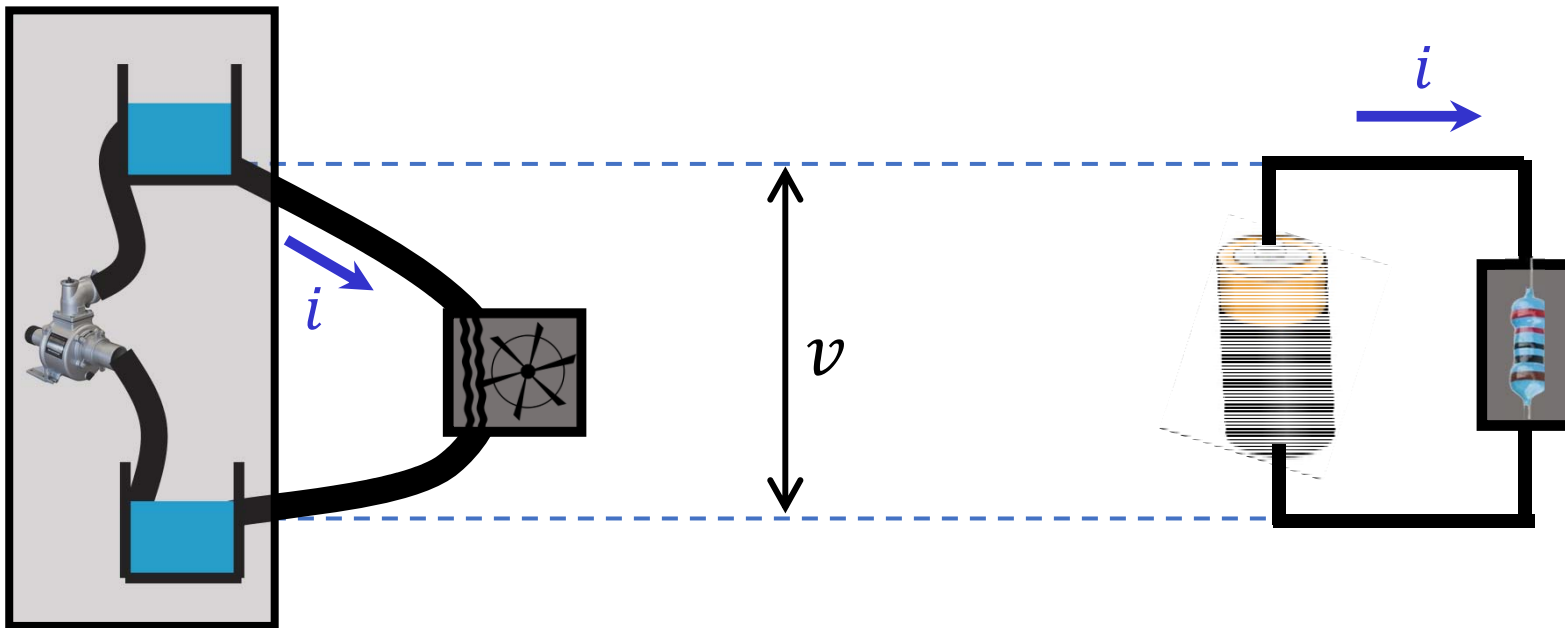



Circuit elements



Same v

Different i

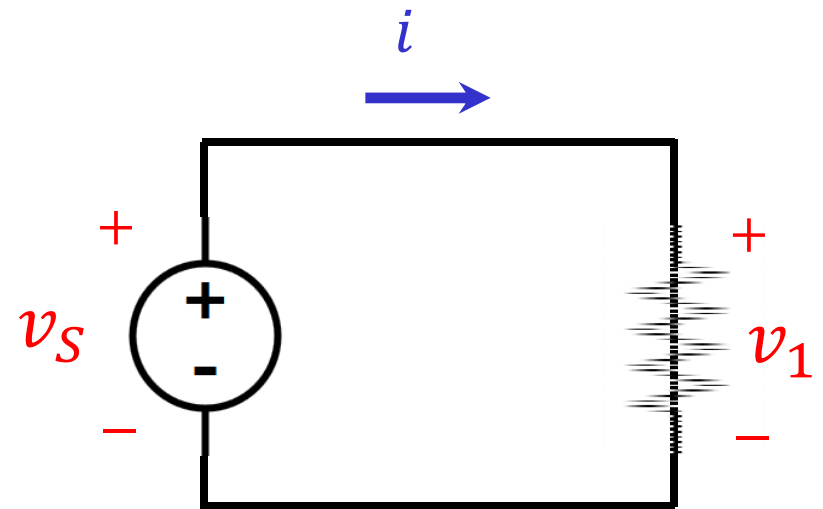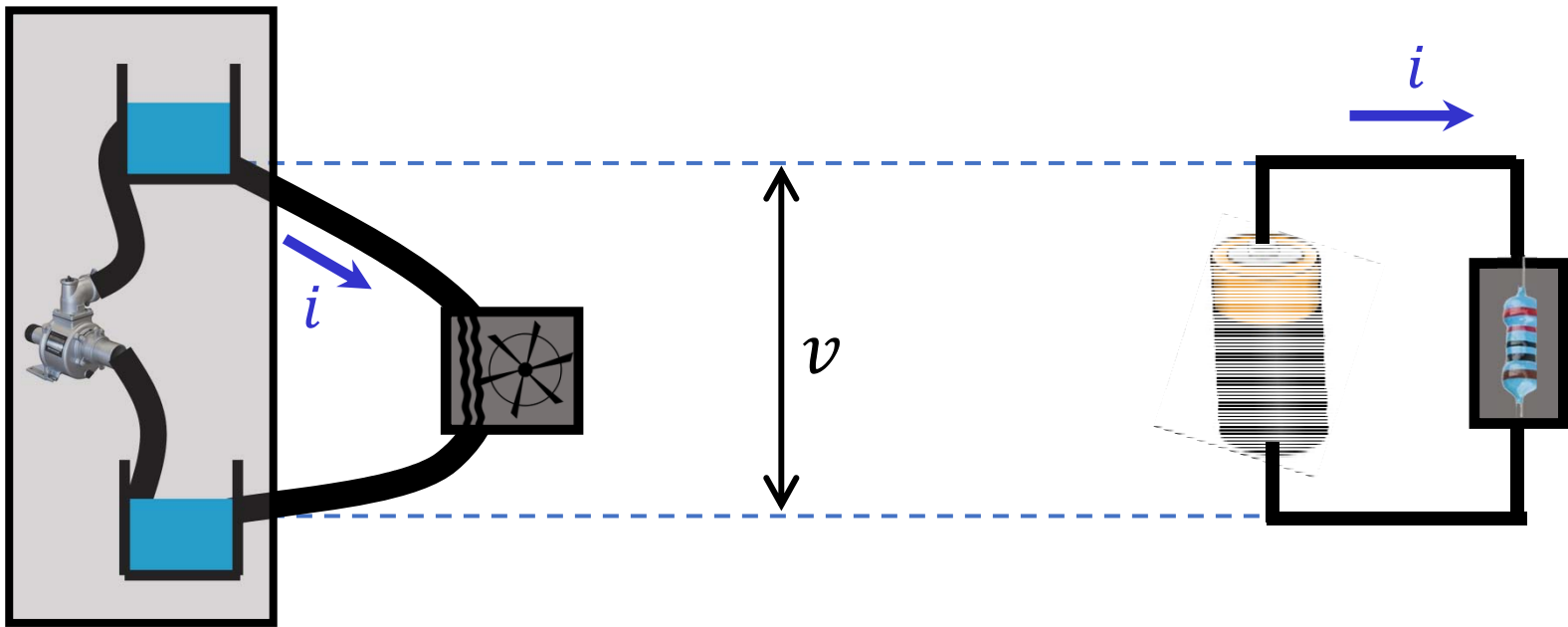

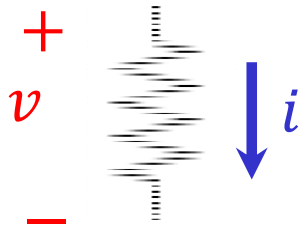

$$v = i \cdot R$$

$$i = \frac{v}{R}$$

Ohm's Law


Resistor

Symbol: R

Unit: ohm (Ω)

For example: 1 k Ω




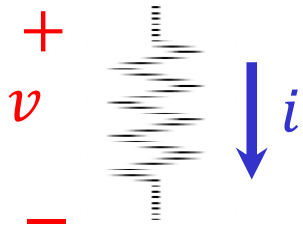

$$v = i \cdot R$$


$$i = \frac{v}{R}$$

Ohm's Law

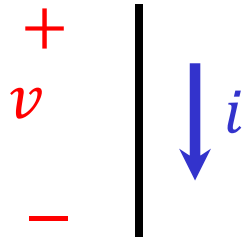

$$v = 0$$


$$R = 0$$

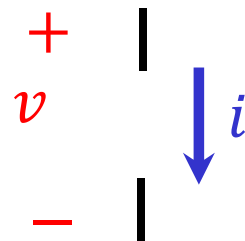

$$i = 0$$


$$R = \infty$$

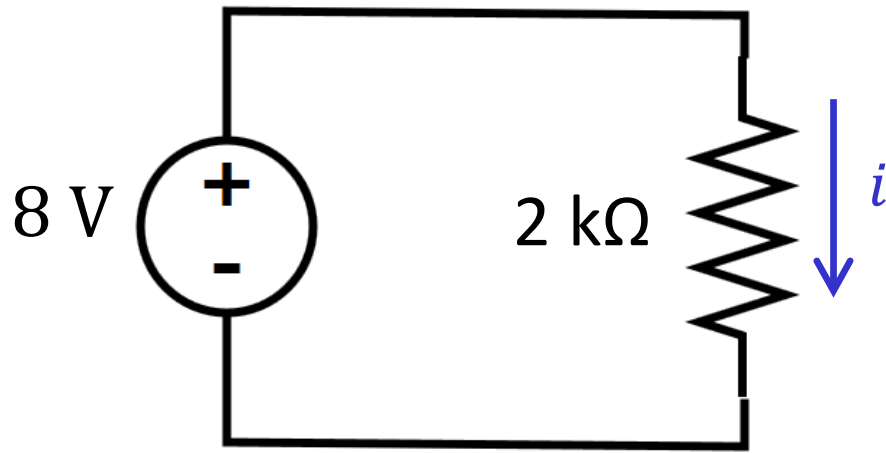If the resistance R is $2\text{ k}\Omega$,
the current i is:





- [A] 0 mA
- [B] 2 mA
- [C] 4 mA
- [D] 16 mA
- [E] I don't know

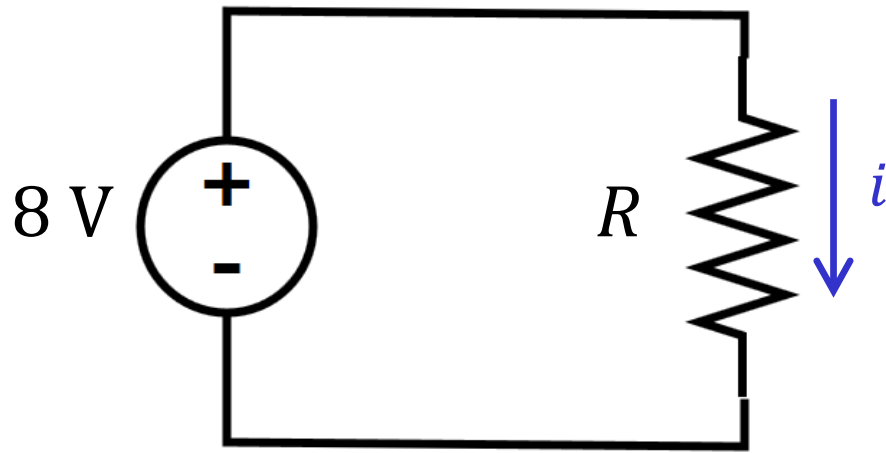What happens when the resistance R is lowered?




- [A] The current i increases
- [B] The current i decreases
- [C] The current i stays the same
- [D] The current i cannot be calculated
- [E] I don't know

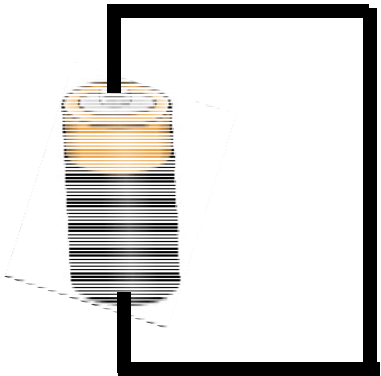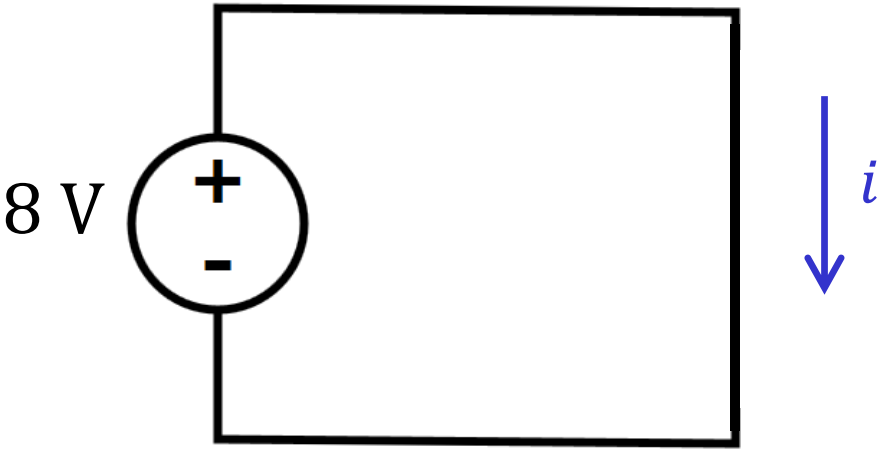What happens when the resistance R is lowered?





Very bad!

What is the current i ?

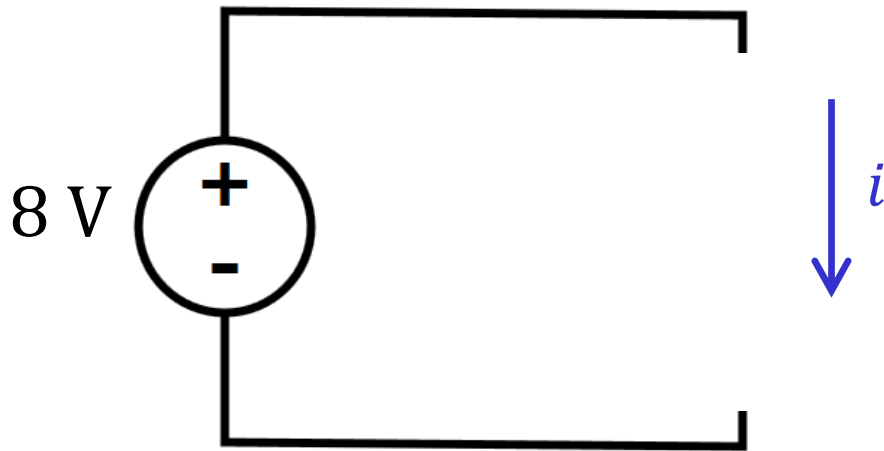


- [A] 0 mA
- [B] 8 mA
- [C] 8 A
- [D] ∞
- [E] I don't know

What is the current i ?

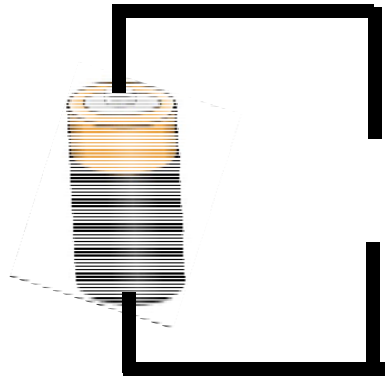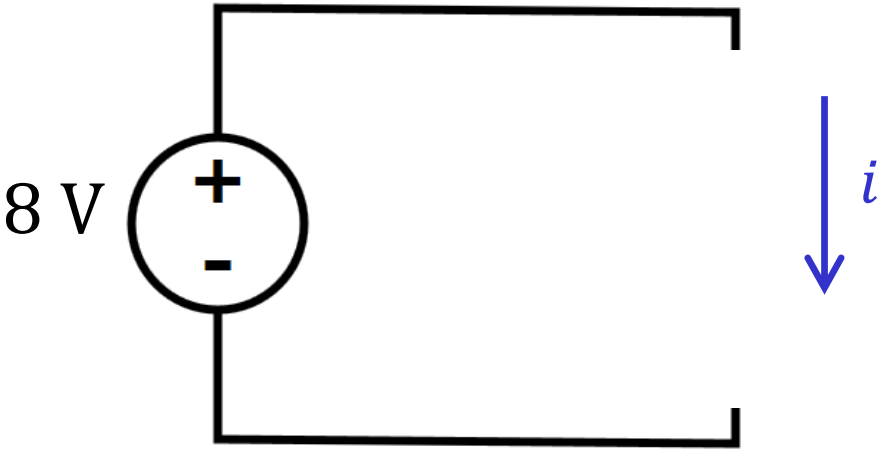




No current

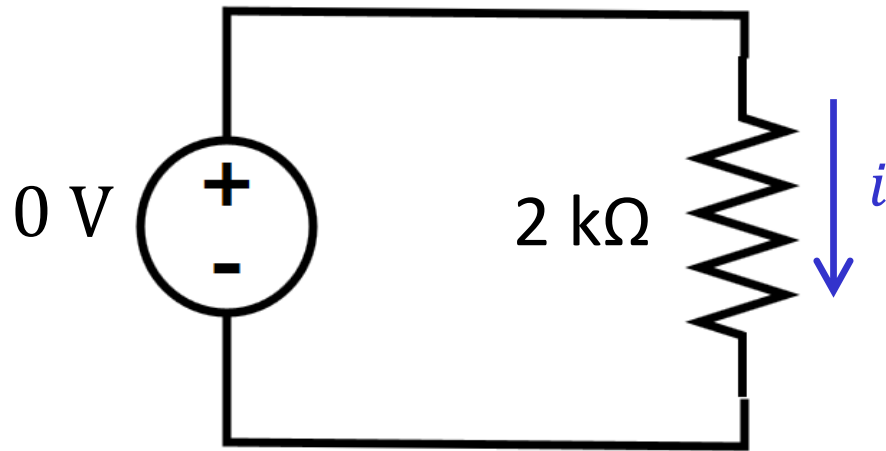If the resistance R is $2\text{ k}\Omega$, the current i is:






- [A] 0 mA
- [B] 2 mA
- [C] 4 mA
- [D] 16 mA
- [E] I don't know


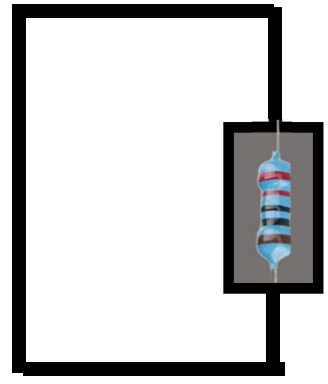
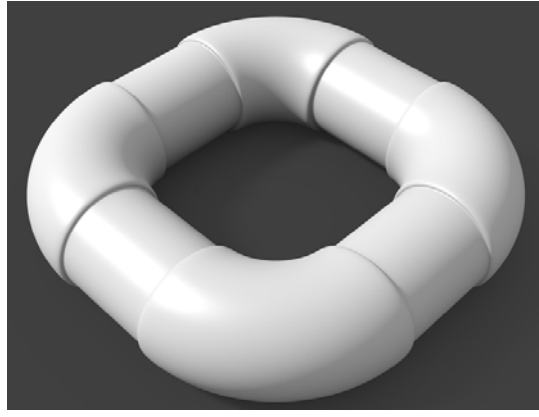
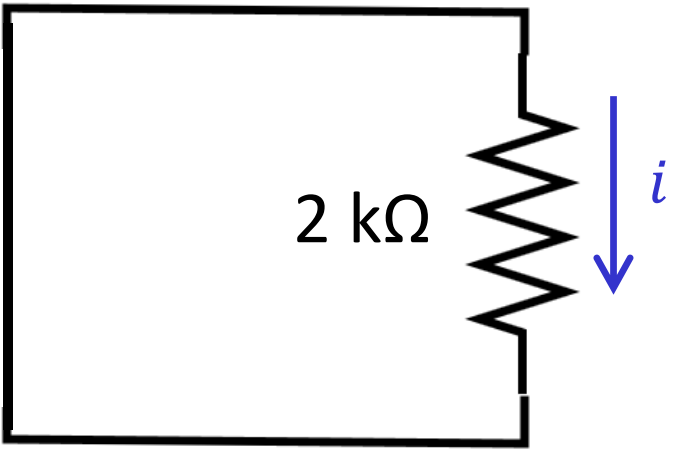
If the resistance R is $2\text{ k}\Omega$, the current i is:




No current

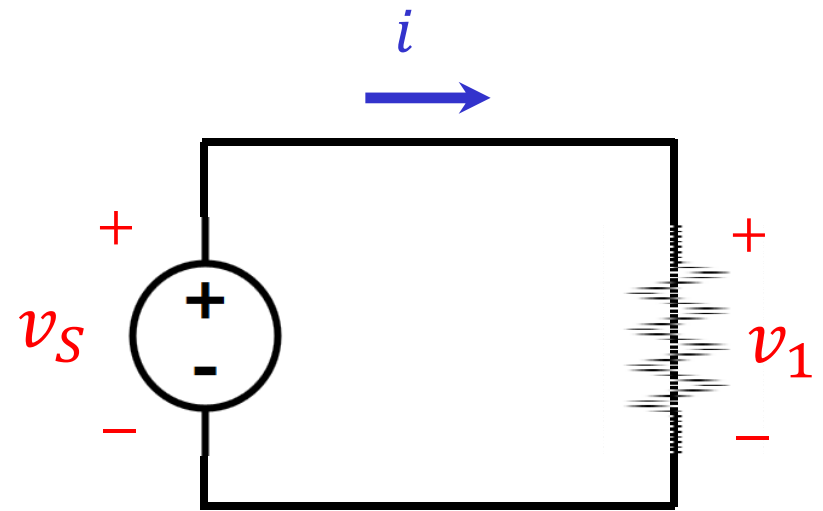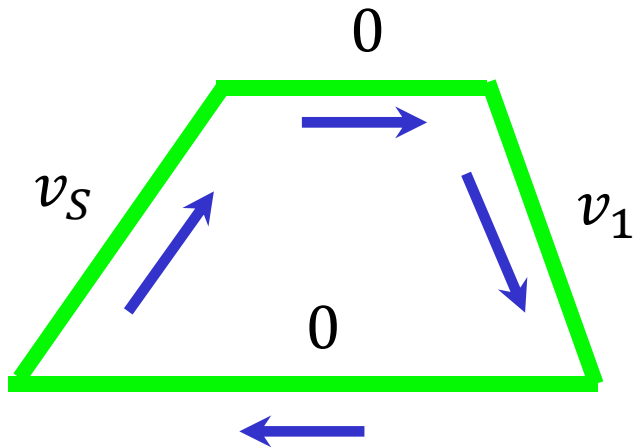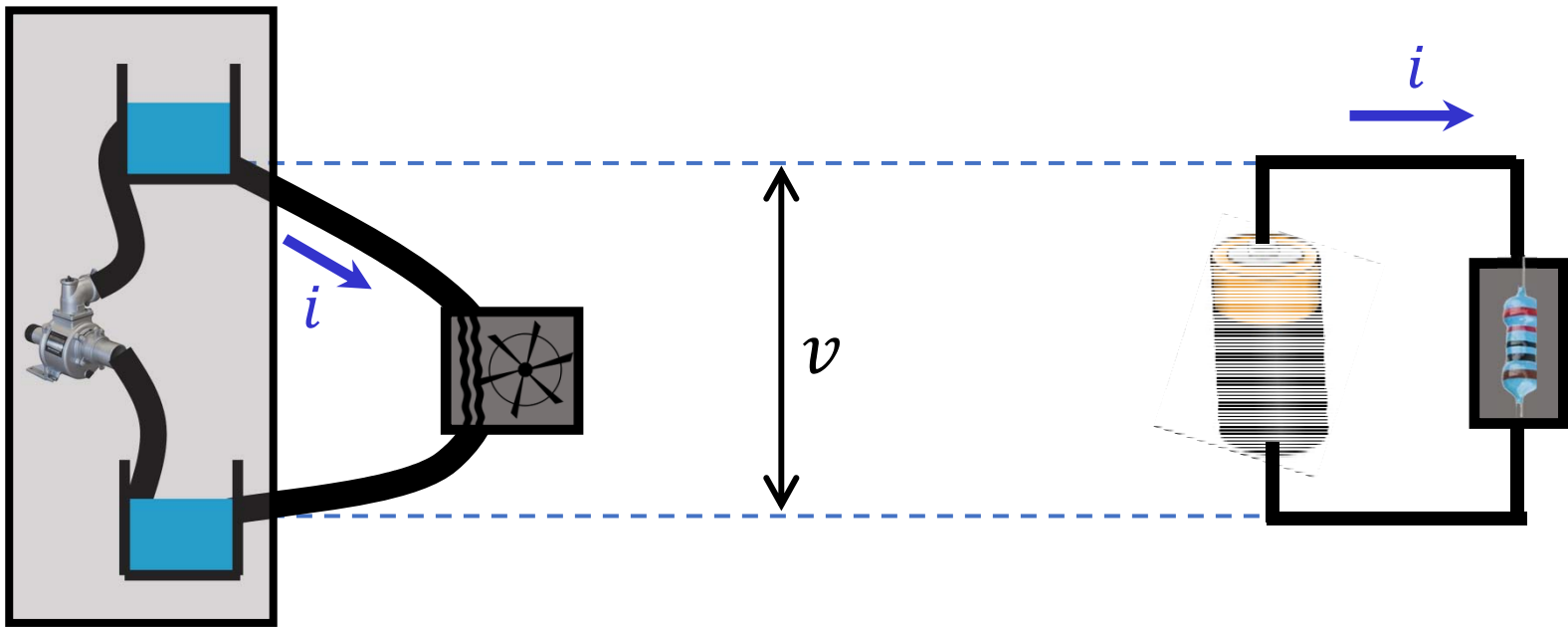

$$v_S = v_1 + v_2$$

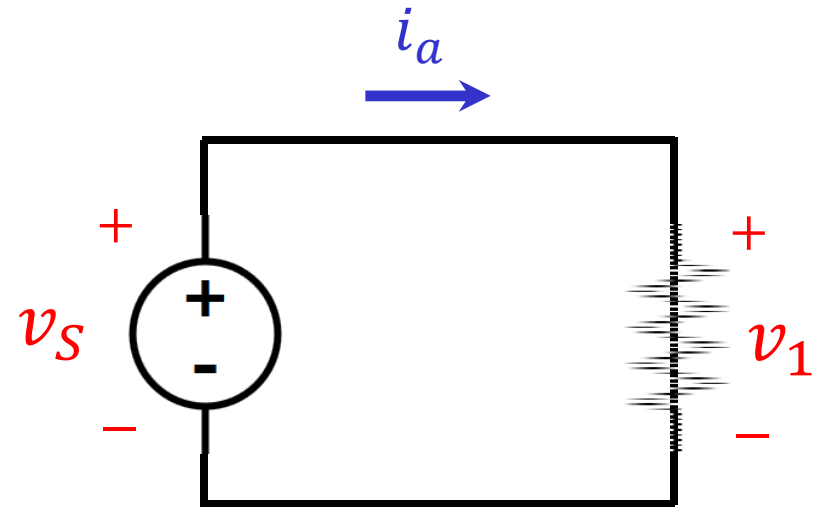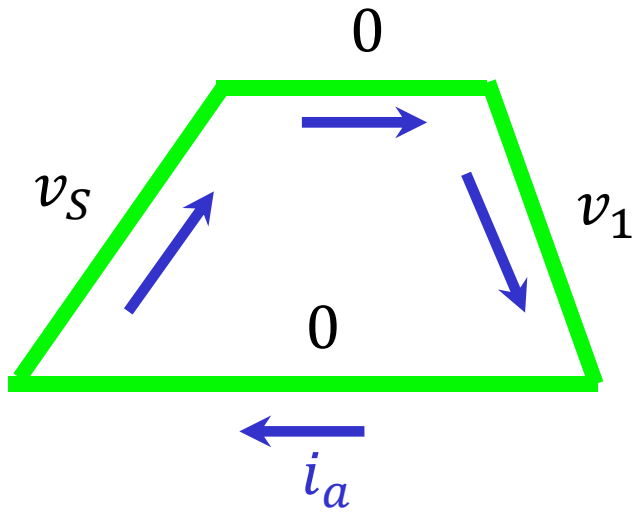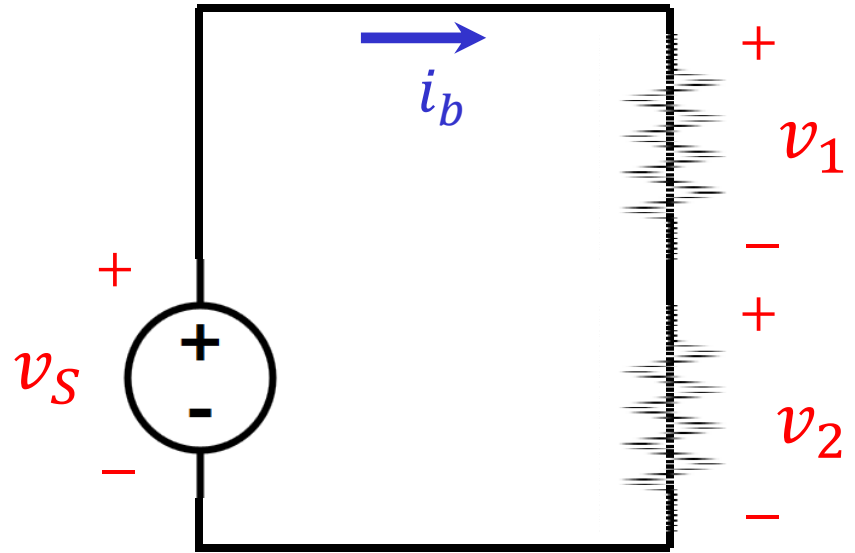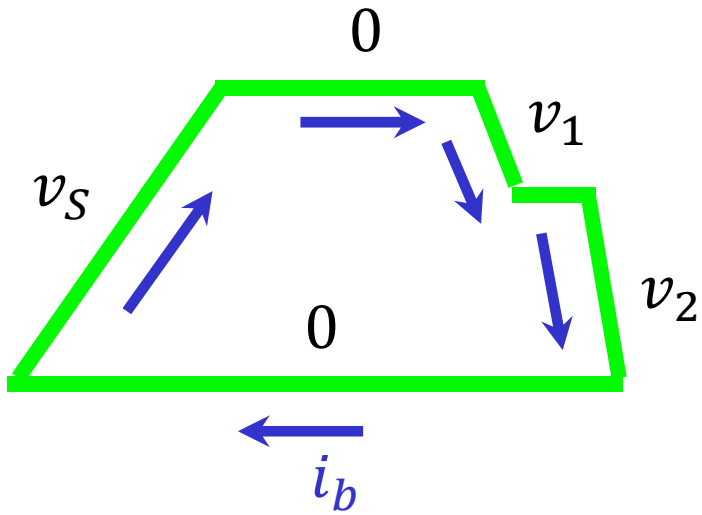


$$v_S = v_1$$

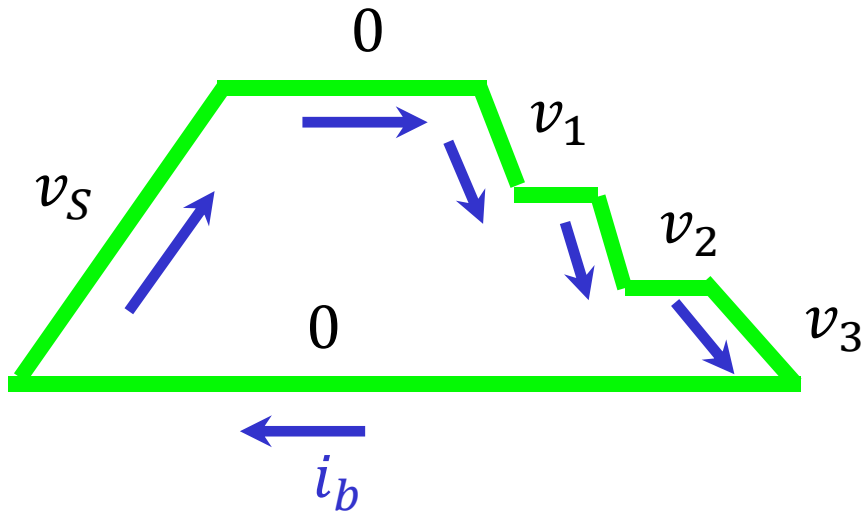


$$\sum_{up} v = \sum_{down} v$$

KVL
Kirchhoff's Voltage Law

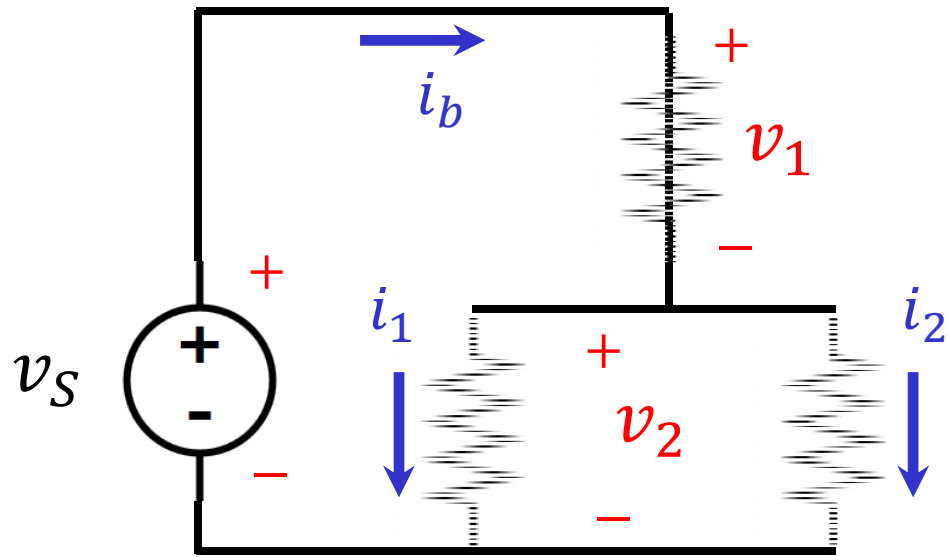



$$i_b = i_1 + i_2$$

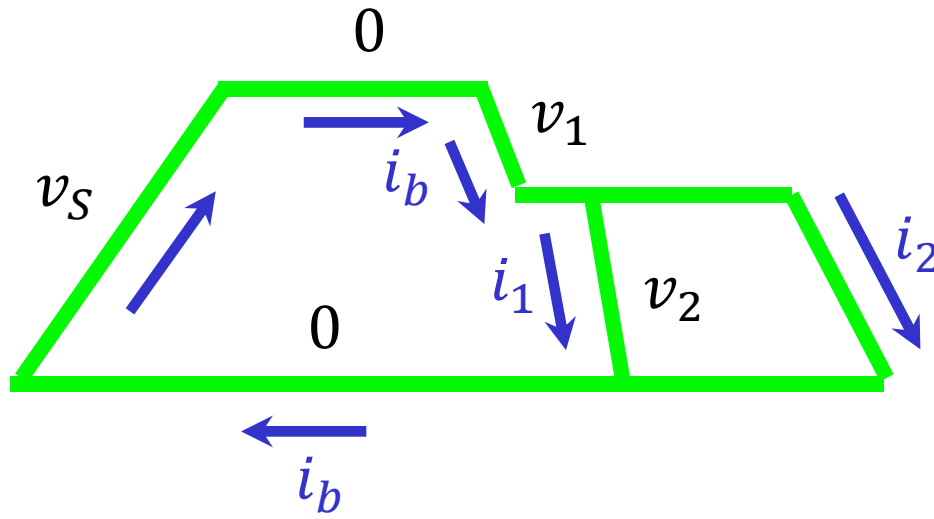

$$\sum_{in} i = \sum_{out} i$$

KCL
Kirchhoff's Current Law

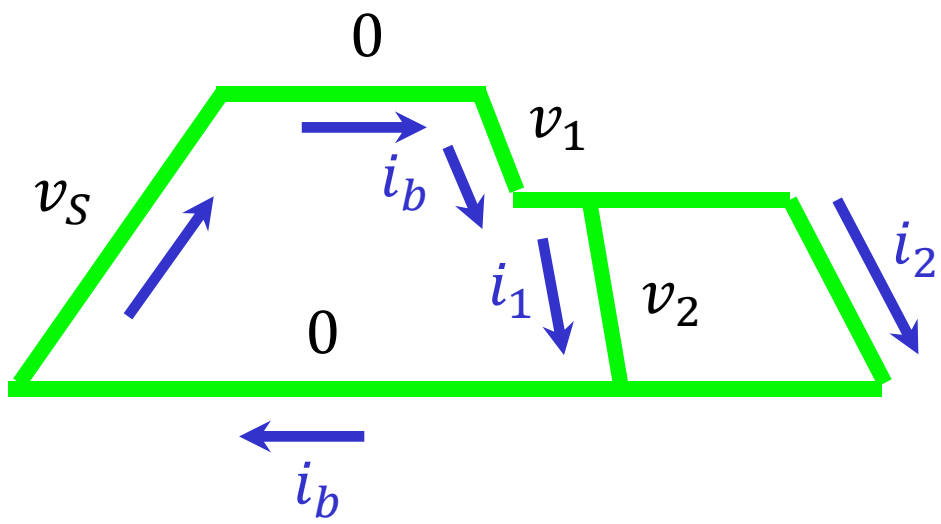


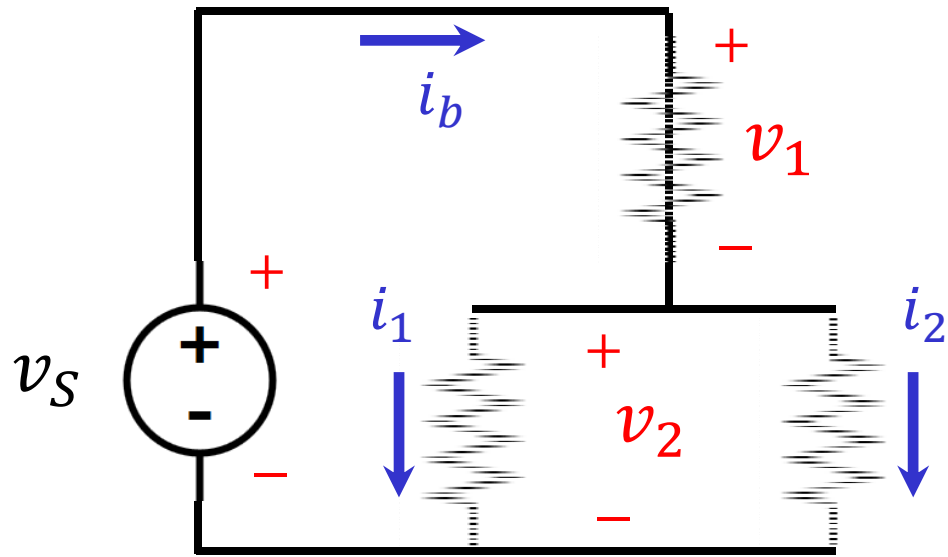



$$v_S = v_1 + v_2$$

$$i_b = i_1 + i_2$$


Relationship
between i and v ?

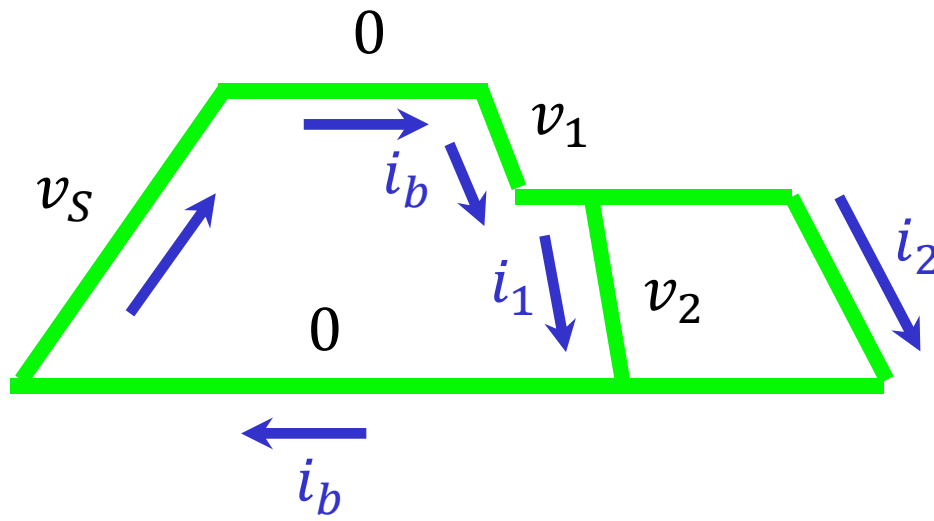

Rules of the game

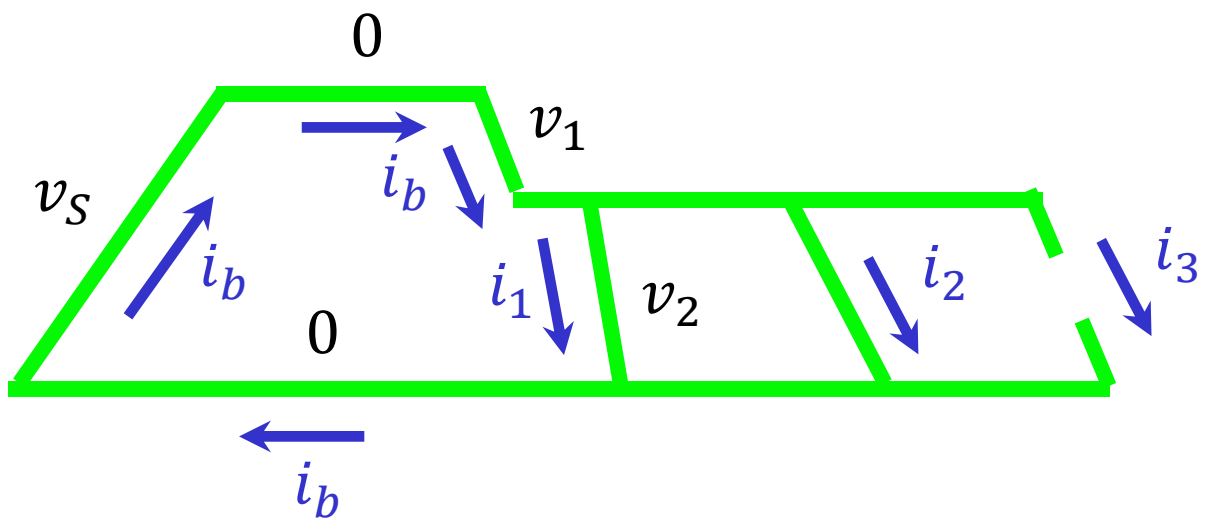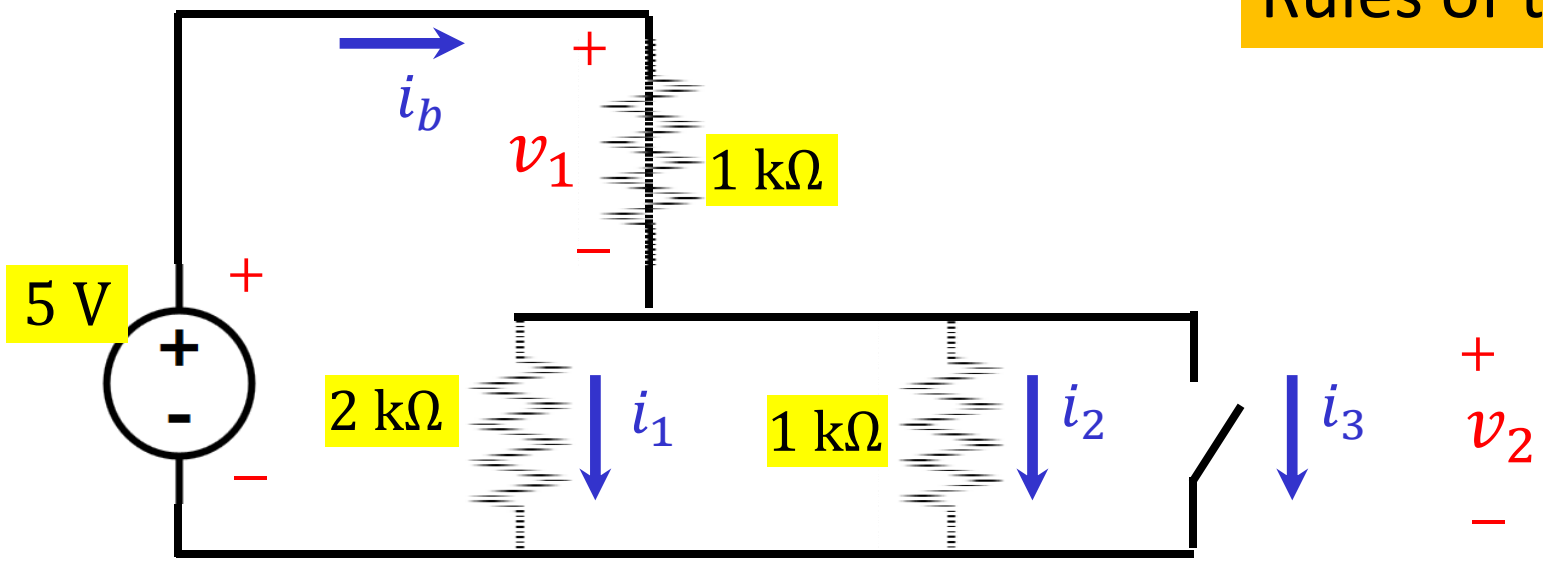

Rules of the game

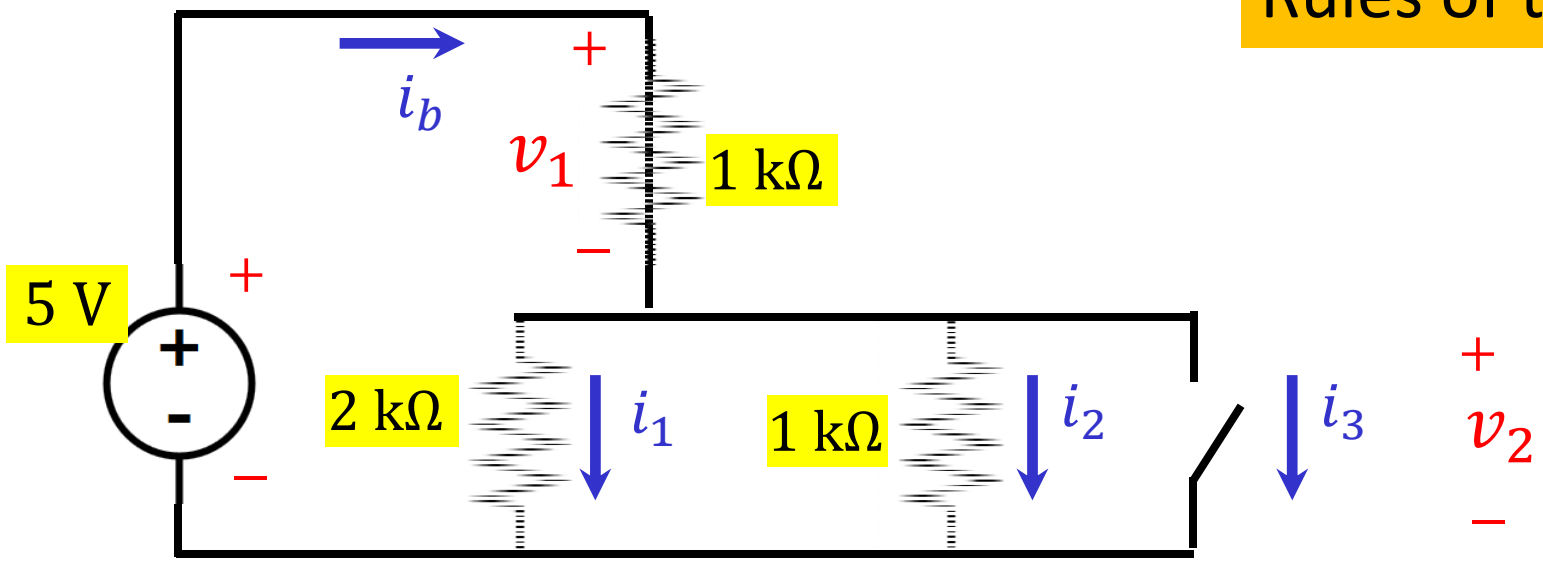

KCL


$$\sum_{in} i = \sum_{out} i$$


KVL

$$\sum_{up} v = \sum_{down} v$$

Ohm's Law


$$v = i \cdot R$$

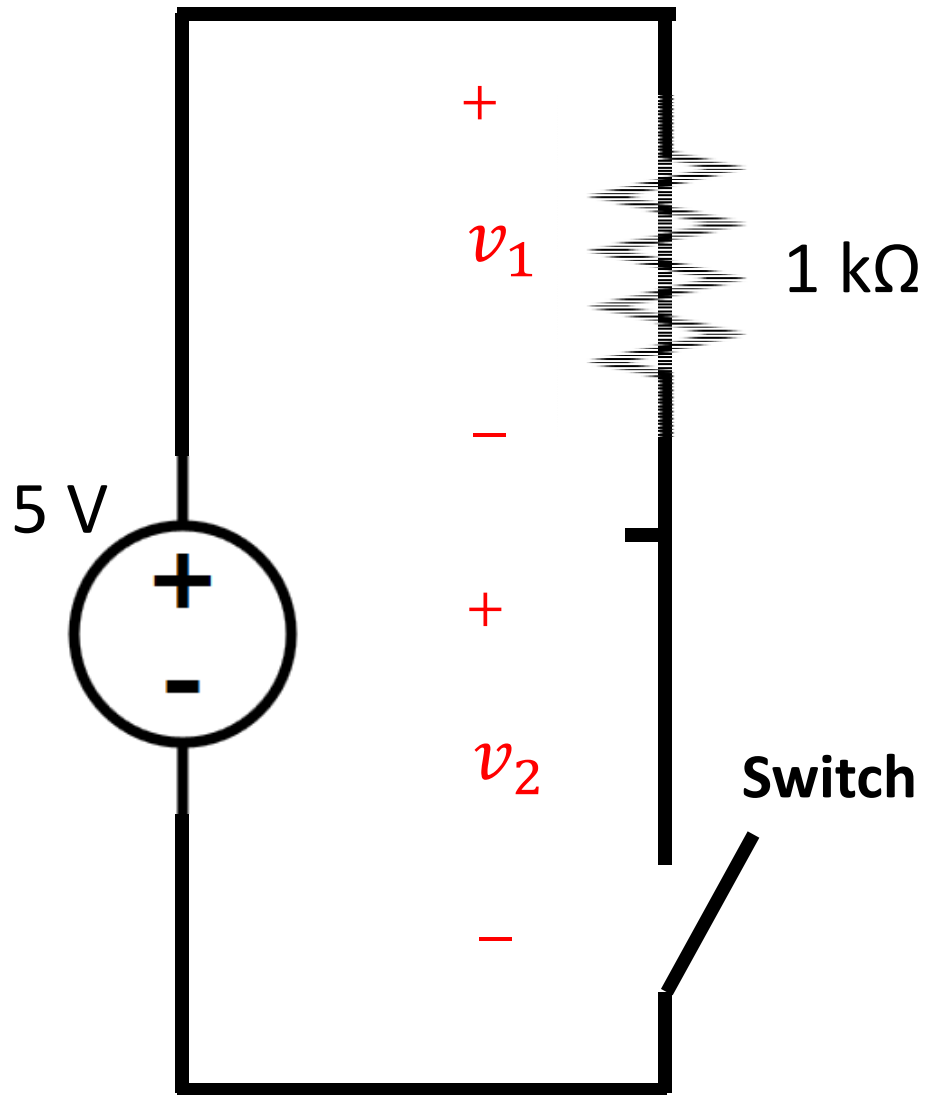

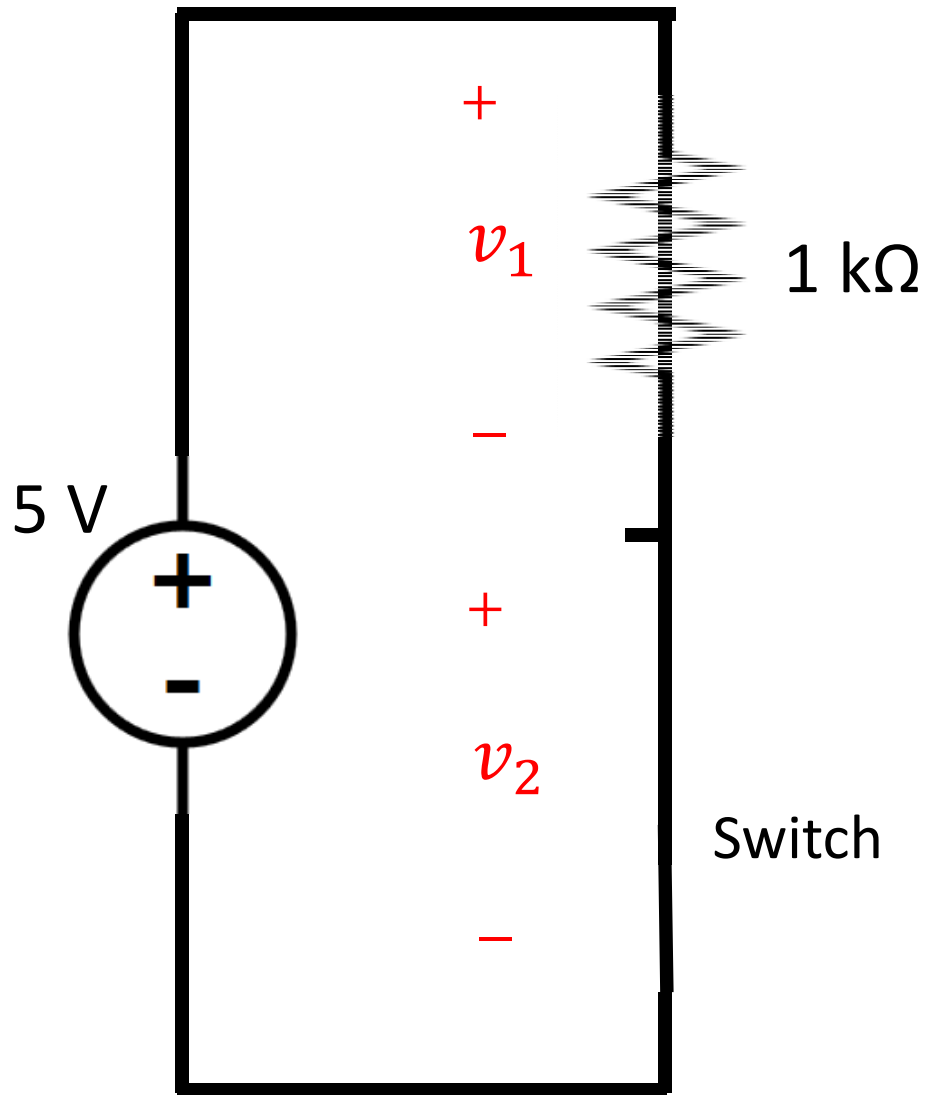


When the switch is closed, the voltage v_2 is:

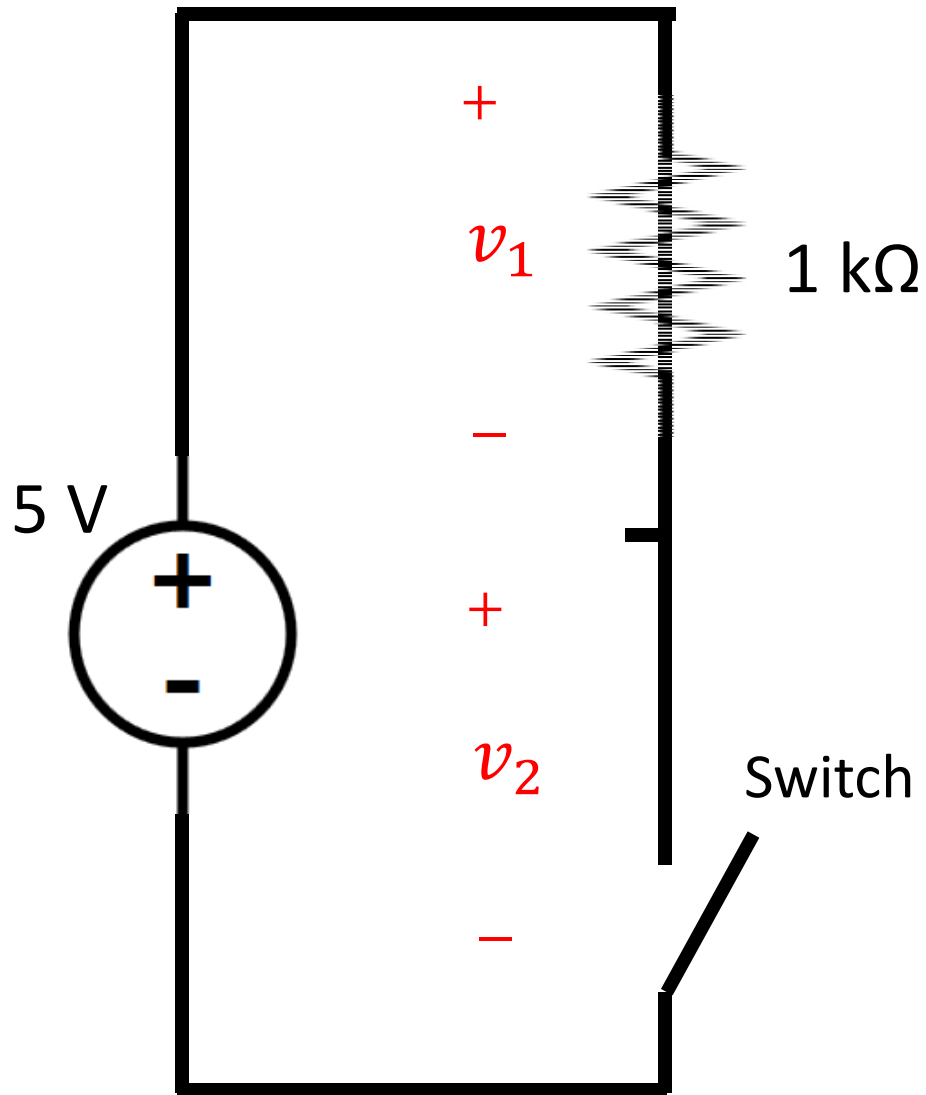- [A] 0 V
- [B] 1 mV
- [C] 1 V
- [D] 4 V
- [E] 5 V



When the switch is open, the voltage v_2 is:

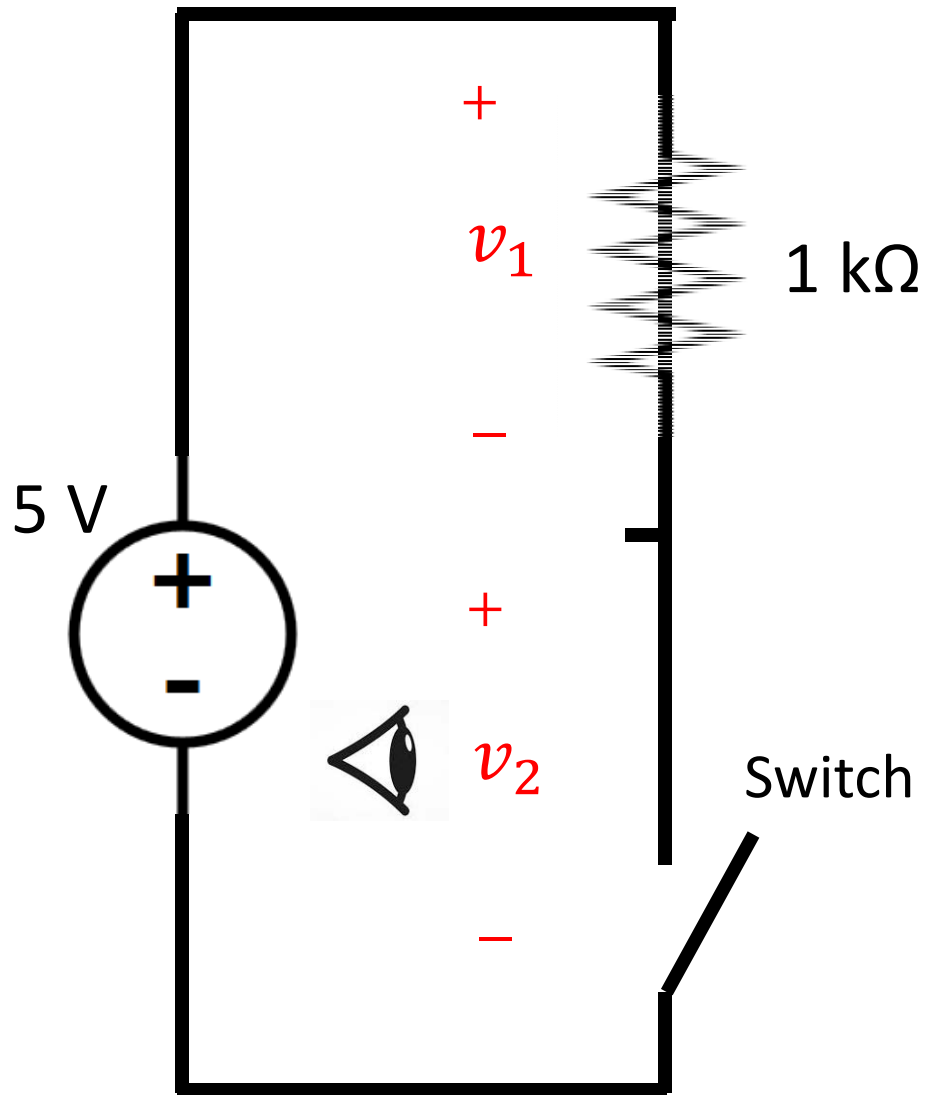
- [A] 0 V
- [B] 1 mV
- [C] 1 V
- [D] 4 V
- [E] 5 V




Observe v_2

HIGH: switch is open
LOW: switch is closed

Observe v_2

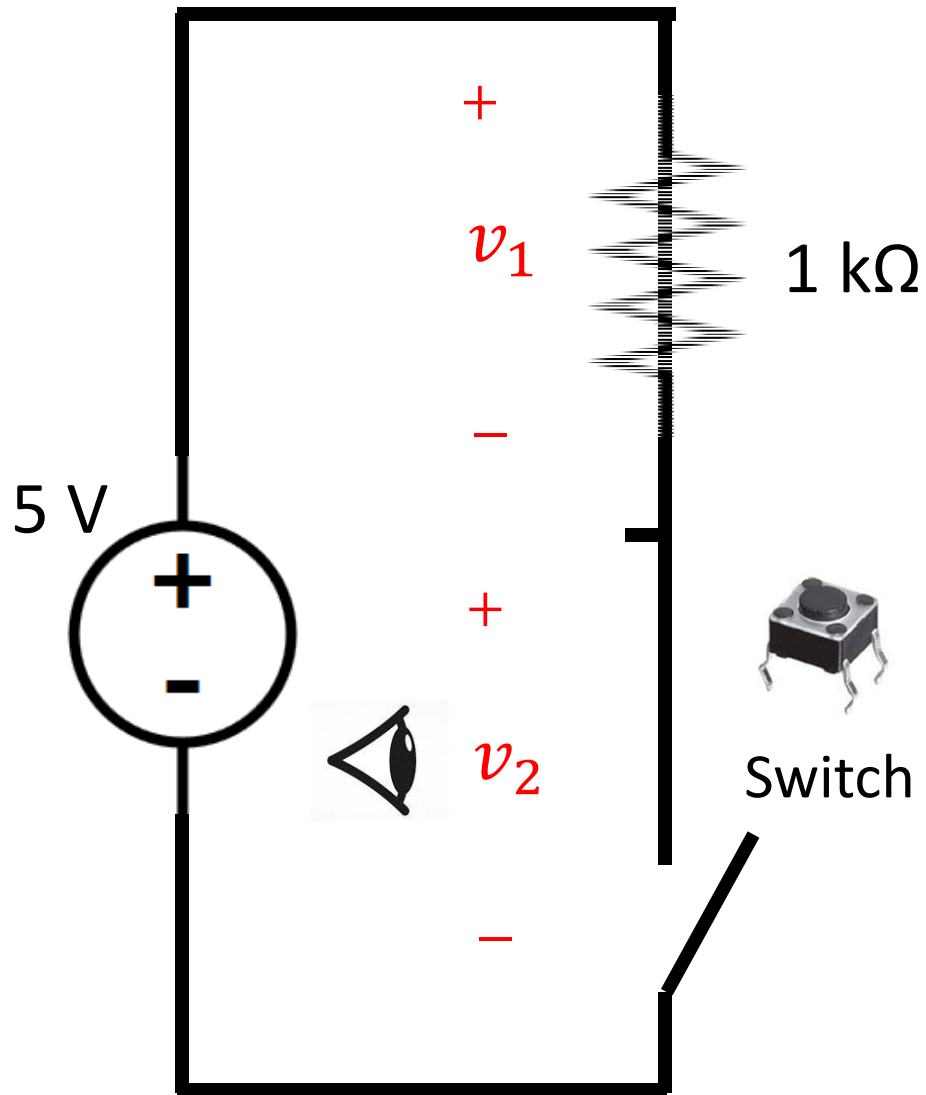


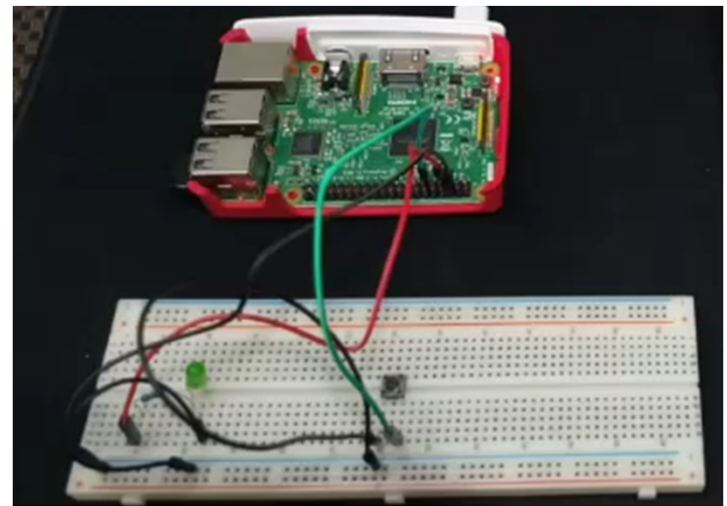HIGH: switch is open
LOW: switch is closed




Other components


$$v = f(i)$$

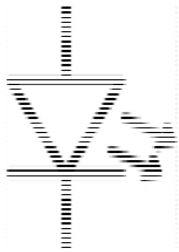

LED

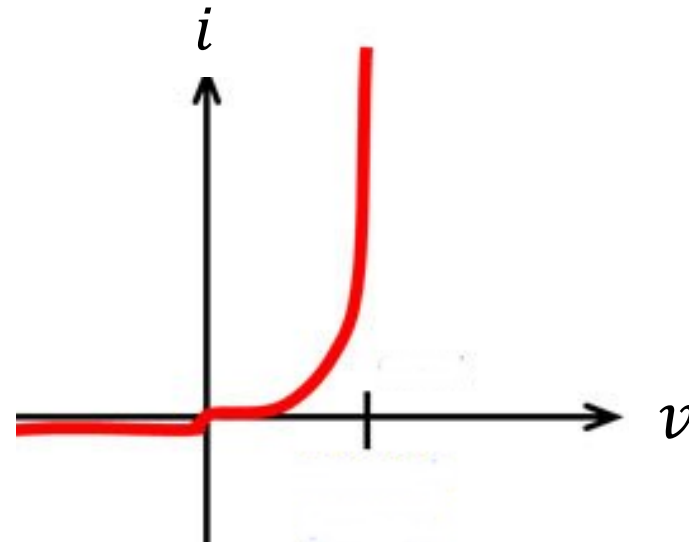


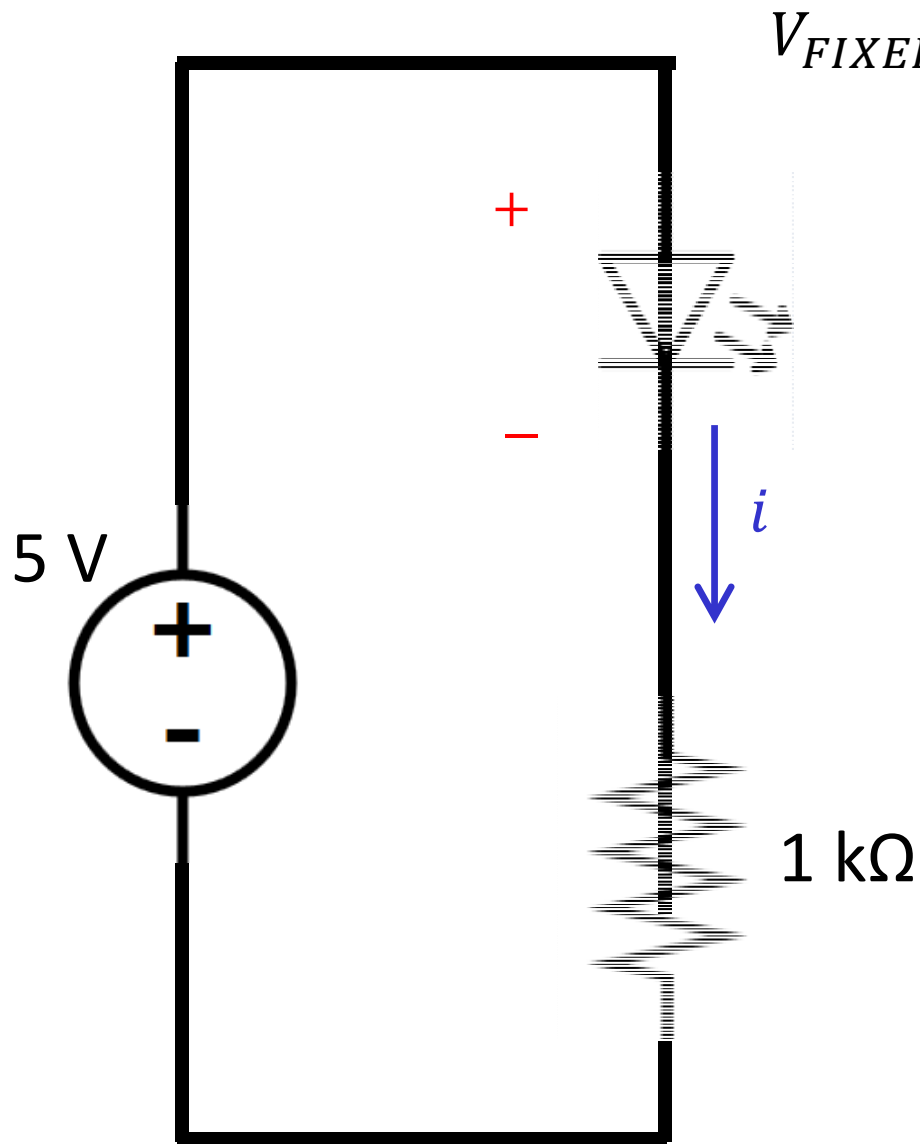Approximation: if there is any (positive) current flowing through it, $v = V_{FIXED}$.
Otherwise, it must be that $v < V_{FIXED}$



1. Assume there is no current
2. Assume there is some current

$$i = 2\text{ mA}$$

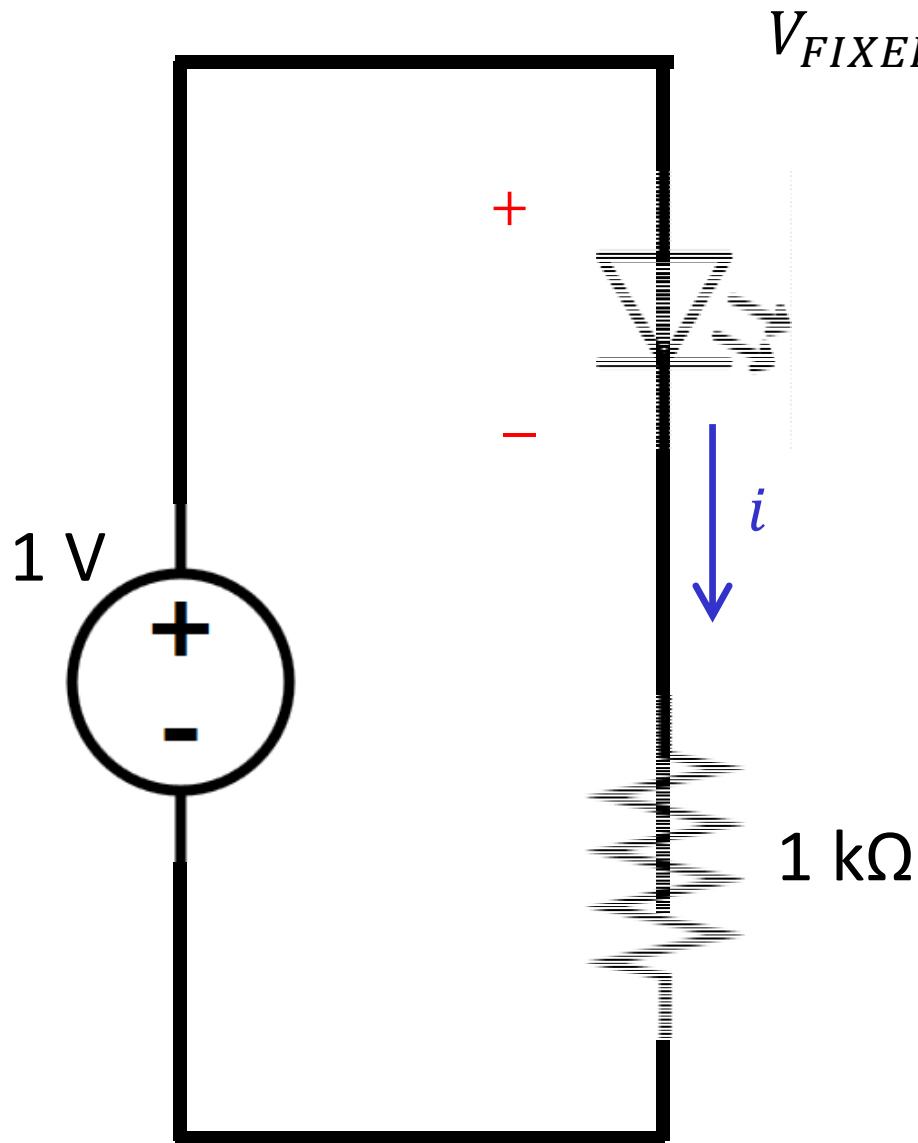

If the voltage over the LED V_{FIXED} is 3V, what is the current i ?

- [A] 0 mA
- [B] 1 mA
- [C] 2 mA
- [D] 3 mA
- [E] 5 mA

Generate V_S

HIGH: light on
LOW: light off

